

# Template Week 2 – Logic

Student number:

## Assignment 2.1: Parking lot

Which gates do you need?

3 AND gates

Complete this table

Parking lot 1	Parking lot 2	Parking lot 3	Result (full)
0	0	0	0
0	0	1	0
0	1	0	0
1	0	0	0
0	1	1	0
1	1	0	0
1	0	1	0
1	1	1	1

## Assignment 2.2: Android or iPhone

Which gates do you need?

1 XOR gate

Complete this table

Android phone	iPhone	Result (Phone in possession)
0	0	0
1	0	1
0	1	1
1	1	0

### Assignment 2.3: Four NAND gates

Complete this table

A	B	Q
0	0	0
1	0	1
0	1	1
1	1	0


How can the design be simplified?

Met een XOR gate aangezien het dezelfde werking heeft en maar 1 gate is.

### Assignment 2.4: Getting to know Logisim evolution

Screenshot of the design with your name and student number in it:


Halil 581687

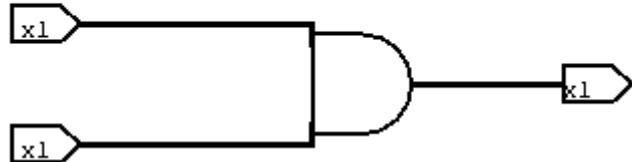

### Assignment 2.5: SR Latch


Screenshot SR Latch in Logisim with your name and student number:

Halil 581687

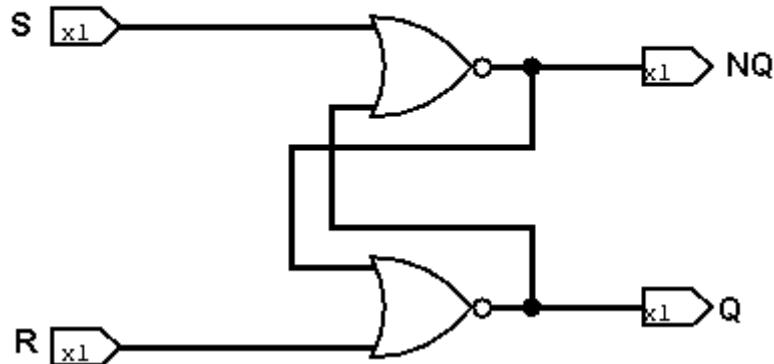
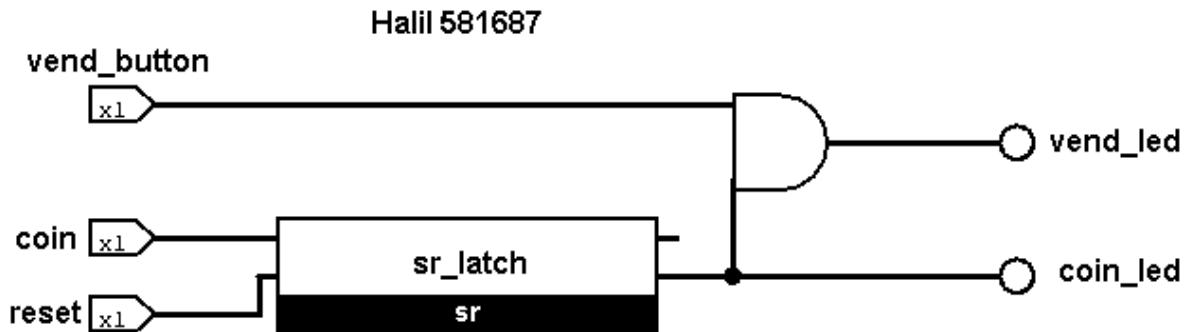
### Assignment 2.6: Vending Machine

Screenshot Vending Machine in Logisim with your name and student number:



### Assignment 2.7: Bitwise operators

Complete the java source code for bitwise operators. Put the source code here.

```
public class Main {  
  
    public static void main(String[] args) {  
  
        evenOdd();  
        powerOfTwo();  
        checkPermissions();  
        assignPermissions();  
        updatePermissions();  
        twosComplement();  
        convertBases();  
    }  
  
    public static void evenOdd() {  
        int number = 5;  
  
        if ((number & 1) == 1)  
            System.out.println(number + " is odd");  
        else  
            System.out.println(number + " is even");  
    }  
  
    public static void powerOfTwo() {  
        int number = 4;  
  
        if (number > 0 && (number & (number - 1)) == 0)  
            System.out.println(number + " is a power of 2");  
        else  
            System.out.println(number + " is NOT a power of 2");  
    }  
}
```

```
public static void checkPermissions() {  
    final int READ = 4;  
    final int WRITE = 2;  
    final int EXECUTE = 1;  
  
    int userPermissions = 7;  
  
    if ((userPermissions & READ) != 0)  
        System.out.println("User has READ permission");  
    else  
        System.out.println("User has NO read permission");  
}  
  
public static void assignPermissions() {  
  
    final int READ = 4;  
    final int WRITE = 2;  
    final int EXECUTE = 1;  
  
    int userPermissions = 0;  
  
    userPermissions |= READ;  
    userPermissions |= EXECUTE;  
  
    System.out.println("User permissions: " + userPermissions);  
}  
  
public static void updatePermissions() {  
  
    final int READ = 4;  
    final int WRITE = 2;  
    final int EXECUTE = 1;  
  
    int userPermissions = 6;  
  
    userPermissions ^= WRITE;  
  
    System.out.println("User permissions: " + userPermissions);  
}  
  
public static void twosComplement() {  
  
    int number = 5;  
    number = ~number + 1;  
  
    System.out.println("Number: " + number);  
}
```

```

public static void convertBases() {

    int number = 10;

    System.out.println("Decimal: " + number);
    System.out.println("Binary: " + Integer.toBinaryString(number));
    System.out.println("Octal: " + Integer.toOctalString(number));
    System.out.println("Hexadecimal: " + Integer.toHexString(number));
}
}

```

#### **Assignment 2.8: Java Application Bit Calculations**

Create a java program that accepts user input and presents a menu with options.

Is number odd?

Is number a power of 2?

Two's complement of number?

Implement the methods by using the bitwise operators you have just learned.

Organize your source code in a readable manner with the use of control flow and methods.

Keep this application because you need to expand it in week 6 for calculating network segments.

```

import java.util.Scanner;

public class Main {

    public static void main(String[] args) {

        Scanner input = new Scanner(System.in);

        System.out.print("Enter a number: ");
        int number = input.nextInt();

        while (true) {

            System.out.println("\n==== MENU ===");
            System.out.println("1. Is number odd?");
            System.out.println("2. Is number a power of 2?");
            System.out.println("3. Two's complement of number?");
            System.out.println("4. Exit");
            System.out.print("Choose: ");

            int choice = input.nextInt();

            if (choice == 1) {
                isOdd(number);
            } else if (choice == 2) {
                isPowerOfTwo(number);
            } else if (choice == 3) {
                twosComplement(number);
            } else if (choice == 4) {
                System.out.println("Exiting...");
                break;
            }
        }
    }
}

```

```

        } else {
            System.out.println("Invalid choice.");
        }
    }

    input.close();
}

public static void isOdd(int number) {
    if ((number & 1) == 1)
        System.out.println(number + " is odd");
    else
        System.out.println(number + " is even");
}

public static void isPowerOfTwo(int number) {
    if (number > 0 && (number & (number - 1)) == 0)
        System.out.println(number + " is a power of 2");
    else
        System.out.println(number + " is NOT a power of 2");
}

public static void twosComplement(int number) {
    int result = ~number + 1;
    System.out.println("Two's complement: " + result);
}
}

```

Ready? Then save this file and export it as a pdf file with the name: [week2.pdf](#)